

Circuit Theory

Problem Set 1

Introduction to Simple Circuits of Resistors

Xin, Wenkang

June 3, 2023

Introduction to Simple Circuits of Resistors

1

$$R = R_1 + R_2 + \frac{1}{1/R_3 + 1/R_4} = 6 \text{ k}\Omega \quad (1)$$

$$I_1 = I_2 = \frac{V_0}{R} = 2 \text{ mA} \quad (2)$$

$$\begin{aligned} V_1 &= I_1 R_1 = 2 \text{ V} \\ V_2 &= I_2 R_2 = 6 \text{ V} \end{aligned} \quad (3)$$

$$\begin{aligned} V_3 &= V_4 = V_0 - V_1 - V_2 = 4 \text{ V} \\ I_3 &= \frac{V_3}{R_3} = 1.3 \text{ mA} \\ I_4 &= \frac{V_4}{R_4} = 0.67 \text{ mA} \end{aligned} \quad (4)$$

•

2

By symmetry, the equivalent circuit consists of three parallel parts (3-6-3) connected in series. The net resistance is:

$$R_{\text{net}} = \frac{R}{3} + \frac{R}{4} + \frac{R}{3} = \frac{5}{6}R \quad (5)$$

•

3

For nodes on the same edge, note that the symmetry of the system demands that the two adjacent nodes to the connection nodes (excluding the other connection node) must have the same potential. Thus any resistors in-between can be treated as parallel. This simplifies the circuit significantly and the eventual result is:

$$R_{\text{net}} = \frac{2}{5}R \quad (6)$$

$$R_{\text{net}} = \frac{7}{12}R \quad (7)$$

For nodes on opposite nodes on the same face, note on this face, the other pair of adjacent nodes must have the same potential. Similarly, the same pair of nodes on the opposite face share the same potential. The result is:

$$R_{\text{net}} = \frac{3}{4}R \quad (8)$$

4

$$V_2 = \frac{R_2}{R_1 + R_2} V_1 = 4 \text{ V} \quad (9)$$

After the load has been applied:

$$V'_2 = \frac{R'}{R_1 + R'} V_1 = 0.95 V_2 \quad (10)$$

where V'_2 is new the voltage drop across R_2 and R' is the net resistance of R_2 and R_L .

Apparently $1/R' = 1/R_2 + 1/R_L$ and:

$$\frac{R'}{R_1 + R'} = 0.95 \frac{R_2}{R_1 + R_2} \quad (11)$$

Solving this equation for R_L yields:

$$R_L = 19 \frac{R_1 R_2}{R_1 + R_2} = 1.52 \text{ k}\Omega \quad (12)$$

•

5

A mesh analysis with passive sign convention yields a system of linear equations:

$$\begin{aligned} 5 - 10I_1 - 20(I_1 + I_2) &= 0 \\ 10 - 15I_1 - 20(I_1 + I_2) &= 0 \end{aligned} \quad (13)$$

Solving the equations yields:

$$\begin{aligned}
 I_1 &= -\frac{1}{26} \text{ A} \\
 I_2 &= \frac{4}{13} \text{ A} \\
 I_3 &= I_1 + I_2 = \frac{7}{26} \text{ A}
 \end{aligned} \tag{14}$$

•

6

Choose the bottom nodes to have zero potential and let the top nodes have potential ϕ . KCL applied at the node above R_2 yields the equation:

$$\frac{\varepsilon - \phi}{R_1} + I_0 = \frac{\phi}{R_2} \tag{15}$$

Solving this gives $\phi = 24 \text{ V}$, which is the potential difference between A and B.

$$\begin{aligned}
 I_1 &= \frac{\phi - \varepsilon}{R_1} = 14 \text{ mA} \\
 I_2 &= \frac{\phi}{R_2} = 24 \text{ mA}
 \end{aligned} \tag{16}$$

Solving this gives $\phi = 6 \text{ V}$, which is the potential difference between A and B.

$$\begin{aligned}
 I_1 &= \frac{\varepsilon - \phi}{R_1} = 4 \text{ mA} \\
 I_2 &= \frac{\phi}{R_2} = 6 \text{ mA}
 \end{aligned} \tag{17}$$

Applying Thevenin's theorem, $R_{\text{eq}} = 1/(1/R_1 + 1/R_2) = 0.5 \text{ k}\Omega$ and $V_{\text{eq}} = \phi = 6 \text{ V}$.
 Applying Norton's theorem, $R_{\text{eq}} = 0.5 \text{ k}\Omega$ and $I_{\text{eq}} = V_{\text{eq}}/R_{\text{eq}} = 12 \text{ mA}$.

•

7

A mesh analysis applied at the central loop yields the equation:

$$V_0 - (I_3 + I_1)R_4 - I_3R_3 - (I_3 + I_2)R_2 - I_3R_1 = 0 \quad (18)$$

Solving this gives $I_3 = -0.8 \text{ mA}$.

Thus:

$$\begin{aligned} I_{R1} &= |I_3| = 0.8 \text{ mA, pointing right} \\ I_{R2} &= |I_3 + I_2| = 3.2 \text{ mA, pointing up} \\ I_{R3} &= |I_3| = 0.8 \text{ mA, pointing left} \\ I_{R4} &= |I_3| = 0.2 \text{ mA, pointing down} \end{aligned} \quad (19)$$