

# Circuit Theory

## Problem Set 3

Complex Impedances and Response of Linear Circuits to AC

Xin, Wenkang

June 3, 2023

# Complex Impedances and Response of Linear Circuits to AC

14

(a)

$$V_{\text{rms}} = V_C \quad (1)$$

(b)

$$V_{\text{rms}} = \frac{V_C}{\sqrt{2}} \quad (2)$$

(c)

$$V_{\text{rms}} = \frac{V_C}{2} \quad (3)$$

(b) and (c) are different because (b) has a higher extreme absolute value.

(d)

$$V_{\text{rms}} = \sqrt{\frac{1}{2T} \int_{-T}^T \left( \frac{V_0}{T} \right)^2 t^2 dt} = \frac{V_0}{\sqrt{3}} \quad (4)$$

•

15

For all the networks we have  $\tilde{V} = V_0 e^{i(\omega t - \pi/2)}$

(a)

$$Z = R - \frac{j}{\omega C} \quad (5)$$

$$\tilde{I} = \frac{\tilde{V}}{Z} = \frac{V_0}{\sqrt{R^2 + (1/\omega C)^2}} e^{i(\omega t - \pi/2 + \phi)} \quad (6)$$

where  $\phi = \tan^{-1} [1/(\omega C R)] = 0.016 \text{ rad}$ .

The current leads the voltage by  $\phi$ .

$$\tilde{V}_R = R \tilde{I} = V_0 \frac{R}{\sqrt{R^2 + (1/\omega C)^2}} e^{i(\omega t - \pi/2 + \phi)} \quad (7)$$

Thus,  $V_{R,\text{max}} = V_0 R / (\sqrt{R^2 + (1/\omega C)^2}) = 10 \text{ V}$ .

(b)

$$Z = j\omega L - \frac{j}{\omega C} \quad (8)$$

$$\tilde{I} = \frac{\tilde{V}}{Z} = \frac{V_0}{\sqrt{(\omega L)^2 + (1/\omega C)^2}} e^{i(\omega t - \pi)} \quad (9)$$

The current lags the voltage by  $\pi/2$ .

$$V_{C,\max} = V_0 \frac{(1/\omega C)}{\sqrt{(\omega L)^2 + (1/\omega C)^2}} = 10 \text{ V} \quad (10)$$

(c)

$$Z = R + j\omega L - \frac{j}{\omega C} \quad (11)$$

$$\tilde{I} = \frac{\tilde{V}}{Z} = \frac{V_0}{\sqrt{R^2 + (\omega L)^2 + (1/\omega C)^2}} e^{i(\omega t - \pi/2 + \phi)} \quad (12)$$

where:

$$\phi = \tan^{-1} \left( \frac{1/(\omega C) - \omega L}{R} \right) = 5.5 \times 10^{-3} \text{ rad} \quad (13)$$

The current leads the voltage by  $\phi$ .

$$V_{L,\max} = V_0 \frac{\omega L}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} = 1.3 \times 10^{-3} \text{ V} \quad (14)$$

(d)

$$Z = \frac{1}{1/R + 1/(j\omega L)} = X e^{i\pi/2} \quad (15)$$

where  $X = 3.95 \Omega$ .

$$\tilde{I} = \frac{\tilde{V}}{Z} = \frac{V_0}{X} e^{i(\omega t - \pi)} \quad (16)$$

The current lags the voltage by  $\pi/2$ .

$$V_{R,\max} = V_0 = 10 \text{ V} \quad (17)$$

(e)

$$Z = \frac{1}{1/(j\omega L) + j\omega C} = Xe^{i\pi/2} \quad (18)$$

where  $X = 39.5 \Omega$ .

$$\tilde{I} = \frac{\tilde{V}}{Z} = \frac{V_0}{X} e^{i(\omega t - \pi)} \quad (19)$$

The current lags the voltage by  $\pi/2$ .

$$V_{C,\max} = V_0 = 10 \text{ V} \quad (20)$$

(f)

$$Z = \frac{1}{1/R + \frac{1}{j\omega L - j/(\omega C)}} = \frac{R(\omega L - 1/(\omega C))}{\sqrt{R^2 + (\omega L - 1/(\omega C))^2}} e^{i\phi} = Xe^{i\phi} \quad (21)$$

where:

$$\phi = \tan^{-1} \left( \frac{R}{1/(\omega C) - \omega L} \right) = -1.54 \text{ rad} \quad (22)$$

$$\tilde{I} = \frac{\tilde{V}}{Z} = \frac{V_0}{X} e^{i(\omega t - \pi/2 - \phi)} \quad (23)$$

The current lags the voltage by  $\phi$ .

$$V_{L,\max} = V_0 \frac{\omega L}{\omega L - 1/(\omega C)} = 10.3 \text{ V} \quad (24)$$

•

## 16

For both circuits,  $\tilde{V}_1 = V_0 e^{i(\omega t - \pi/2)}$ .

(I)

$$\tilde{V}_2 = \tilde{V}_1 \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{V_0}{\sqrt{1 + (\omega CR)^2}} e^{i(\omega t - \pi/2 - \phi)} \quad (25)$$

where:

$$\phi = \tan^{-1} (\omega CR) \quad (26)$$

$$\frac{V_{2,\max}}{V_{1,\max}} = \frac{1}{\sqrt{1 + (\omega CR)^2}} \quad (27)$$

(II)

$$\tilde{V}_2 = \tilde{V}_1 \frac{j\omega L}{R + j\omega L} = \frac{V_0}{\sqrt{1 + (R/\omega L)^2}} e^{i(\omega t - \pi/2 + \phi)} \quad (28)$$

where:

$$\phi = \tan^{-1} \left( \frac{R}{\omega L} \right) \quad (29)$$

$$\frac{V_{2,\max}}{V_{1,\max}} = \frac{1}{\sqrt{1 + (R/\omega L)^2}} \quad (30)$$

For both circuits, the ratio is given by:

$$\frac{1}{\sqrt{1 + (\omega/\omega_0)^2}} \quad (31)$$

and the phase is given by:

$$\tan^{-1} \left( \frac{\omega}{\omega_0} \right) \quad (32)$$

•

**17**We have  $\tilde{I} = I_0 e^{i(\omega t - \pi/2)}$ .

(a)

$$\tilde{V}_C = \frac{\tilde{I}}{j\omega C} = \frac{I_0}{\omega C} e^{i(\omega t - \pi)} \quad (33)$$

where  $\frac{I_0}{\omega C} = 10 \text{ V}$ .

$$\tilde{V}_L = \tilde{I} j\omega L = I_0 \omega L e^{i\omega t} \quad (34)$$

where  $I_0 \omega L = 20 \text{ V}$ .

$$\tilde{V}_R = \tilde{I} R = I_0 R e^{i(\omega t - \pi/2)} \quad (35)$$

where  $I_0 R = 10 \text{ V}$ .

$$\tilde{V} = I_0 X e^{i(\omega t - \pi/2 + \phi)} \quad (36)$$

where:

$$X = \sqrt{R^2 + (\omega L - 1/(\omega C))^2} = 141 \Omega \quad (37)$$

and:

$$\phi = \tan^{-1} \left( \frac{\omega L - 1/(\omega C)}{R} \right) = \pi/2 \quad (38)$$

and  $I_0 X = 14.1 \text{ V}$

(b)

$$P = \text{Re}(\tilde{V}) \text{Re}(\tilde{I}) = I_0^2 X \sin(\omega t + \phi) \sin \omega t \quad (39)$$

(c)

$$W_L = \frac{1}{2} L \text{Re}(\tilde{I})^2 = \frac{1}{2} L I_0^2 \sin^2 \omega t \quad (40)$$

$$W_C = \frac{1}{2} C \text{Im}(\tilde{V}_C)^2 = \frac{1}{2} \frac{1}{\omega^2 C} I_0^2 \cos^2 \omega t \quad (41)$$

(d) Their maximum values are  $\frac{1}{2} L I_0^2$  and  $\frac{1}{2} \frac{1}{\omega^2 C} I_0^2$  respectively.

(f) For the sum to be constant,  $L = 1/(\omega^2 C) = 0.1 \text{ mH}$ .

•

## 18

For this circuit:

$$Z = R + j\omega L - \frac{j}{\omega C} = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} e^{i\phi} \quad (42)$$

For the amplitude to be minimum:

$$\frac{d}{d\omega} \left[ \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} \right] = \frac{2(\omega L - \frac{1}{\omega C})(L + \frac{1}{\omega^2 C})}{2\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = 0 \quad (43)$$

This happens when  $\omega L - \frac{1}{\omega C} = 0$  or  $\omega = \frac{1}{\sqrt{LC}}$ . Then  $Z = Re^{i\phi}$ , and  $V_{C,\max} = V_0/(\omega CR) = 3.16 \text{ V}$ . •

**19**

$$Z = j\omega L - \frac{j}{2\omega C} + \frac{1}{j\omega C + \frac{1}{\frac{1}{2j\omega C} + j\omega L}} = j \left( \omega L - \frac{1}{2\omega C} - \frac{1}{\omega C + \frac{2\omega C}{1-2\omega^2 CL}} \right) = 0 \quad (44)$$

Solving this equation (avoiding the asymptote) gives  $\omega = \sqrt{5/(2LC)}$ . The other root  $\omega = \sqrt{1/(2LC)}$  is obtained by substituting the asymptote value directly into the original expression. •

**20**

(a) For the bridge to be balanced:

$$Z_1 \frac{1}{\frac{1}{R_4} + j\omega C_4} = \frac{1}{j\omega C_3} R_2 \quad (45)$$

Solving for  $Z_1$  yields:

$$Z_1 = R_2 \frac{C_4}{C_3} - j \frac{R_2}{R_4} \frac{1}{\omega C_3} \quad (46)$$

(b) For a series combination:

$$R_1 - j \frac{1}{\omega C_1} = R_2 \frac{C_4}{C_3} - j \frac{R_2}{R_4} \frac{1}{\omega C_3} \quad (47)$$

so that  $R_1 = R_2 C_4 / C_3$  and  $C_1 = C_3 R_4 / R_2$ .

(c) For a parallel combination:

$$\frac{1}{\frac{1}{R_1} + j \frac{1}{\omega C_1}} = R_2 \frac{C_4}{C_3} - j \frac{R_2}{R_4} \frac{1}{\omega C_3} \quad (48)$$

Solving this equation yields:

$$\begin{aligned} R_1 &= \frac{R_2 [1 + (\omega C_4 R_4)^2]}{\omega^2 C_3 C_4 R_4^2} \\ C_1 &= \frac{C_3 R_4}{R_2 [1 + (\omega C_4 R_4)^2]} \end{aligned} \quad (49)$$

•

**21**

(a) Note that  $\omega_0 L = 1/(\omega_0 C) = \sqrt{3}R$

$$Z = R + \frac{1}{\frac{1}{R+j\omega_0 L} + \frac{1}{R-j/(\omega_0 C)}} = R + \frac{(R+j\sqrt{3}R)(R-j\sqrt{3}R)}{2R} = 3R \quad (50)$$

(b)

$$V_{AX} = \frac{R}{3R} V_{AB} = \frac{V_{AB}}{3} \quad (51)$$

$$V_{XY} = \frac{2}{3} V_{AB} \frac{R}{R+j\sqrt{3}R} = \frac{V_{AB}}{3} e^{i\pi/3} \quad (52)$$

$$V_{XZ} = \frac{1}{3} V_{AB} \frac{R}{R-j/(\sqrt{3}R)} = \frac{V_{AB}}{3} e^{-i\pi/3} \quad (53)$$

•

**22**

We have:

$$V_{xy} = \left( \frac{1}{2} - \frac{1}{1+j\omega RC} \right) V = \frac{j\omega RC - 1}{j\omega RC + 1} \frac{V}{2} \quad (54)$$

so the amplitude is  $|V_{xy} = V/2|$  which is independent of  $R$  and the phase is  $\pi - 2\phi$  where  $\phi = \tan^{-1}(\omega RC)$ .

Therefore, when  $R = 1/(\omega C)$ ,  $\pi - 2\phi = \pi/2$ .